

**CHAPTER 2:..... TABLE OF CONTENTS:**

<b>2. BINARY AND LOGIC OPERATIONS.....</b>	<b>2</b>
2.1 EXERCISE CREATE AN AND GATE PROGRAM .....	2
2.2 EXERCISE CREATE AN OR GATE PROGRAM .....	2
2.3 EXERCISE CREATE A OR BEFORE AND PROGRAM.....	3
2.4 EXERCISE CREATE A AND BEFORE OR PROGRAM.....	3
2.5 EXERCISE CREATE A START STOP PROGRAM .....	4
2.6 EXERCISE .....	5
2.6.1 Exercise: Set-Up AND and NAND.....	5
2.6.2 Exercise: Set-Up a Garage Three Bay Shed.....	5
2.7 CHECK WHAT YOU'VE LEARNT THIS CHAPTER.....	6
I Know: .....	6
I Can:.....	6

**TABLE OF FIGURES:**

ELECTRICAL SERIES CIRCUIT AND CONTROL SYSTEM OVERVIEW .....	2
AND GATE CONTROL PROGRAM .....	2
ELECTRICAL PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW .....	2
OR GATE CONTROL PROGRAM .....	2
ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW .....	3
OR BEFORE AND GATE CONTROL PROGRAM.....	3
ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW.....	3
AND BEFORE OR GATE CONTROL PROGRAM.....	3
ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW.....	4
OPTION 1 MOTOR START / STOP CONTROL PROGRAM.....	4
OPTION 2 MOTOR START / STOP USING A FLAG CONTROL PROGRAM .....	4
OPTION 3 MOTOR START / STOP USING A CONNECTOR CONTROL PROGRAM .....	4
AND AND NAND CONTROL PROGRAM .....	5
THREE BAY HORSE SHED CONTROL PROGRAM.....	5

## 2. Binary and Logic Operations.


Complete the following exercises using the LOGO Function Block Diagram (FBD) Format to get familiar with the LOGO software. For each exercise complete the following:

- Save the Program in the Sub-folder LOGO.
- Test the Program using the LOGO Tools → Simulation.
- Use the following Addresses; S1 = I1, S2 = I2, S3 = I3, K1 = Q1

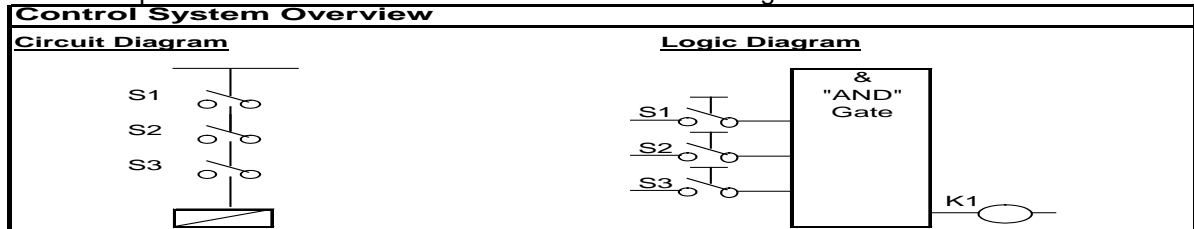
### 2.1 Exercise Create an AND Gate Program

- Create a User Program which energises K1 when the switches S1, S2 and S3 are energised.
- Name the Program as AND Gate Logic.

This corresponds with the series electrical circuit and with the logic “AND” function



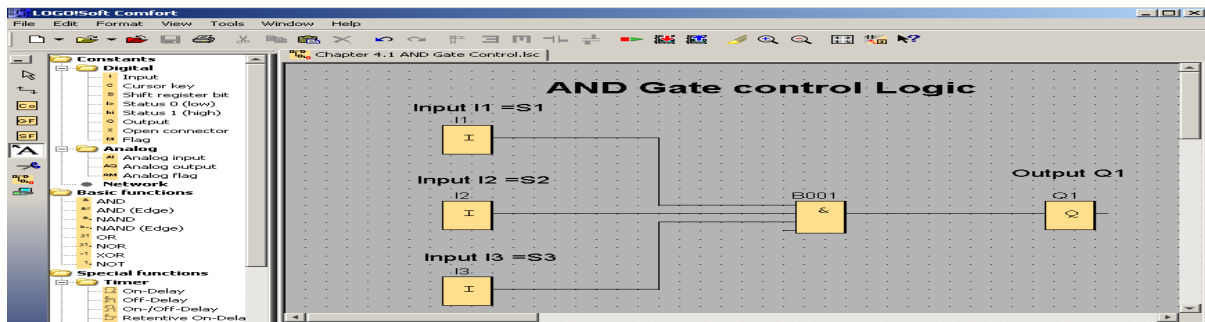ELECTRICAL SERIES CIRCUIT AND CONTROL SYSTEM OVERVIEW




AND GATE CONTROL PROGRAM

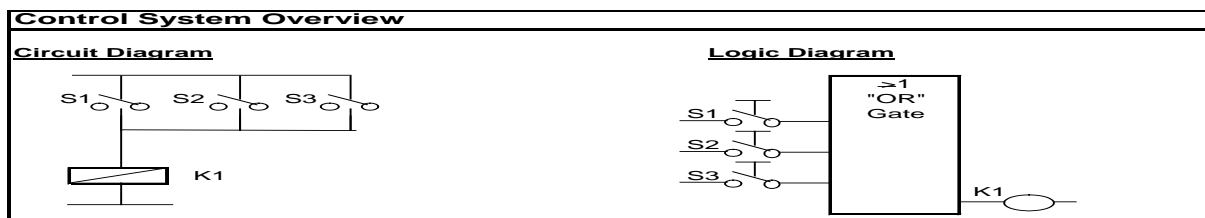
### 2.2 Exercise Create an OR Gate Program

- Create a User Program which energises K1 when switches S1 or S2 or S3 are energised.
- Name the Program as OR Gate Logic.

This corresponds with the Parallel electrical circuit and with the logic “OR” function



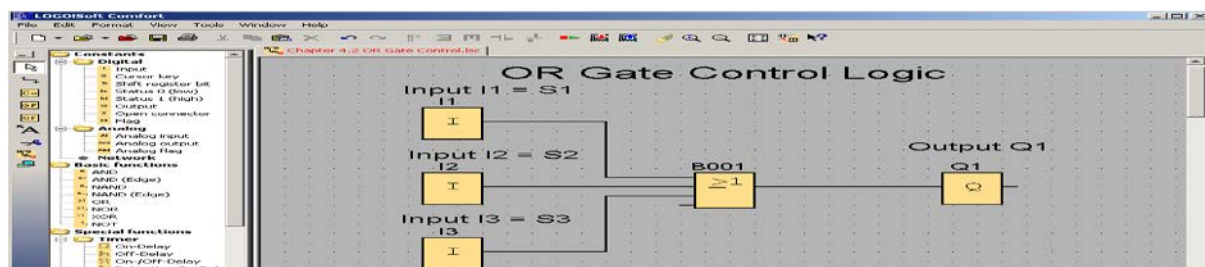ELECTRICAL PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW




OR GATE CONTROL PROGRAM

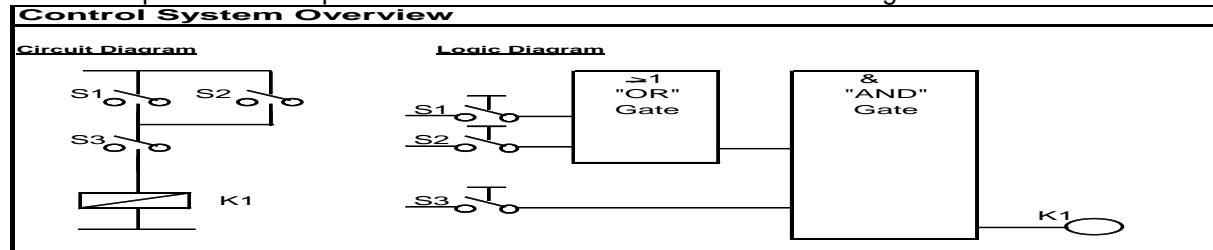
## 2.3 Exercise Create a OR Before AND Program

- Create a User Program which energises K1 when switches S1 or S2 and S3 are closed.
- Name the Program as OR Before AND.

This corresponds with the parallel & series electrical circuit and with the logic **OR** before the **AND**.



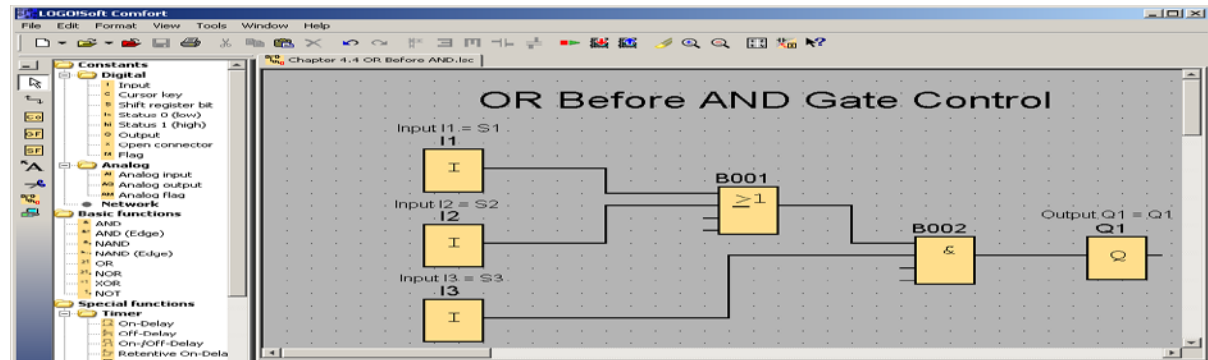ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW




OR BEFORE AND GATE CONTROL PROGRAM

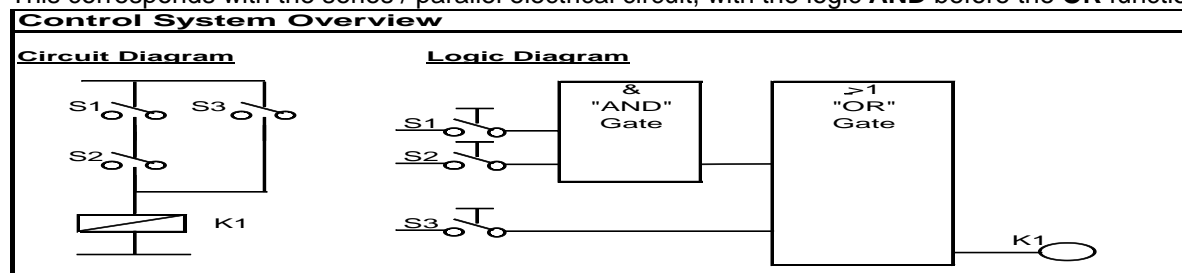
## 2.4 Exercise Create a AND Before OR Program

- Create a User Program which energises K1 when switches S1 and S2 or S3 are closed.
- Name the Program as AND Before OR.

This corresponds with the series / parallel electrical circuit, with the logic **AND** before the **OR** function.



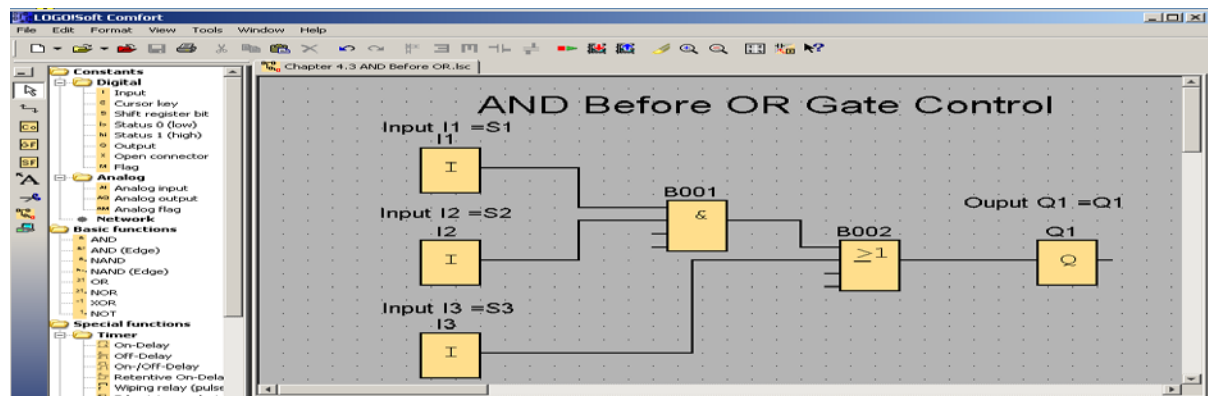ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW




AND BEFORE OR GATE CONTROL PROGRAM

## 2.5 Exercise Create a START STOP Program

- Create a User Program which energises K1 when switch S1 (Start PB) is pressed, provided S2 (Healthy Stop) is healthy.
- Name the Program as AND Before OR.


This is a typical standard Start/Stop electrical circuit used for motor control whereby pushbuttons are used for starting S1 (**Normally Open Contact**) and pushbutton S2 (Normally Closed Contact) to stop the motor. This is often called a **LATCH On** or **HOLD On** circuit.

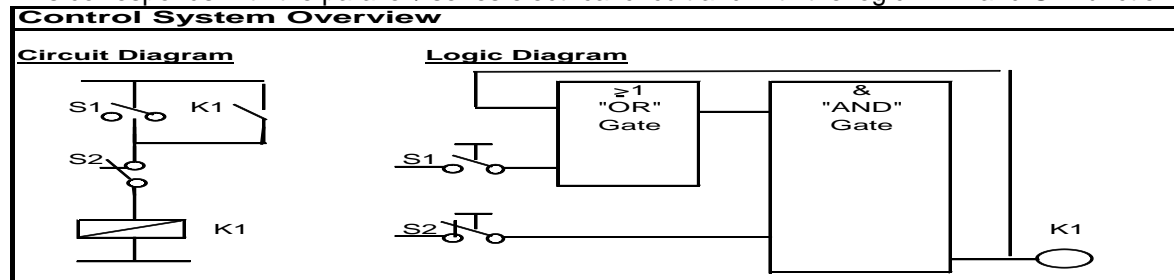This corresponds with the parallel / series electrical circuit and with the logic **AND** and **OR** function.




### ELECTRICAL SERIES & PARALLEL CIRCUIT AND CONTROL SYSTEM OVERVIEW

#### Option 1 Standard Solution

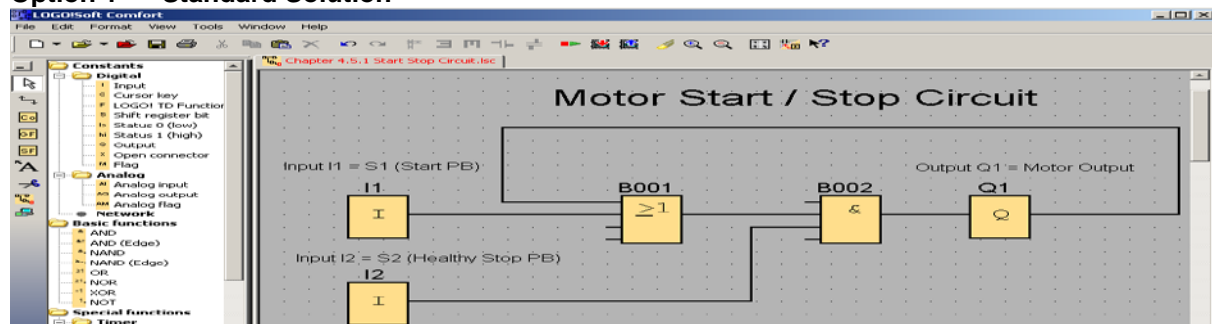


OPTION 1 MOTOR START / STOP CONTROL PROGRAM

#### Option 2: Solution Using a Flag

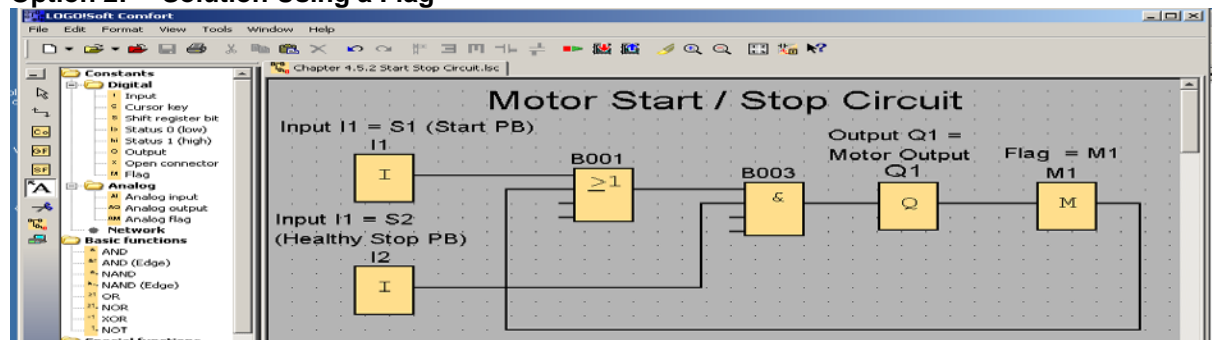

OPTION 2 MOTOR START / STOP USING A FLAG CONTROL PROGRAM

#### Option 2: Solution Using a Flag

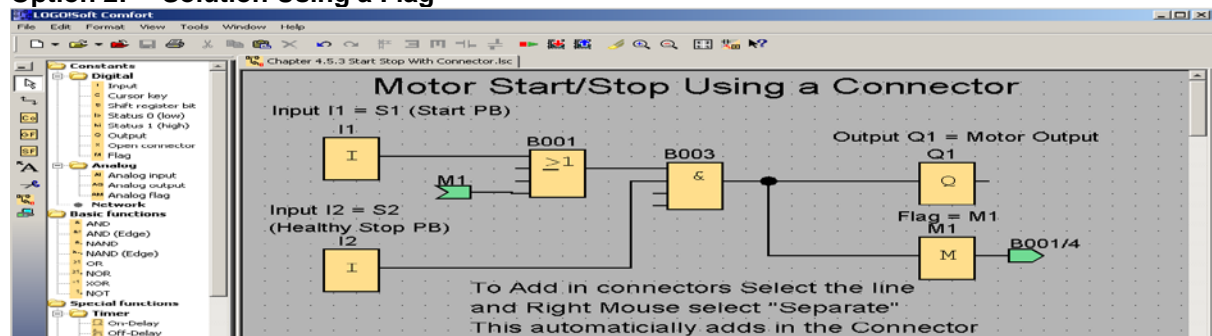

OPTION 3 MOTOR START / STOP USING A CONNECTOR CONTROL PROGRAM


## 2.6 Exercise

Are we limited in the number of times we can test an input in a User Program ?

A pushbutton type control switch has a break (Normally Closed) contact. Does it provide a signal (a) when it is depressed or (b) when it is untouched and explain ?
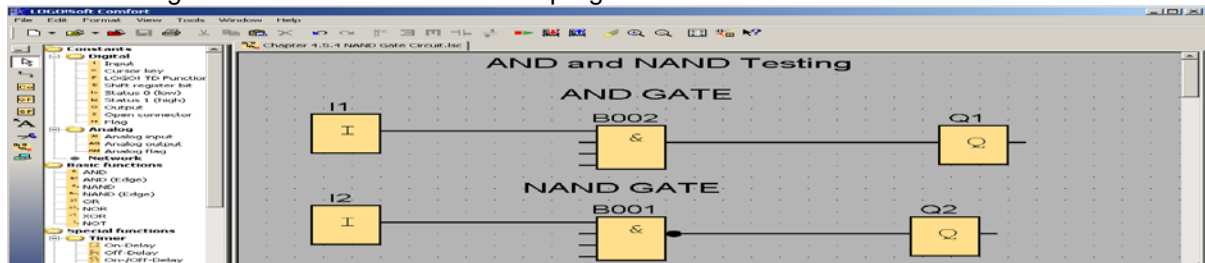
### 2.6.1 Exercise: Set-Up AND and NAND

- Complete the following as outlined below.
- Save the program as **AND and NAND Gate Control** and download it to the CPU.
- Debug and Test the **AND and NAND** program.



AND AND NAND CONTROL PROGRAM

when it is status of Q1 when S1 is not pressed and explain ?, \_\_\_\_\_  
 when it is status of Q2 when S2 is not pressed and explain ?, \_\_\_\_\_

### 2.6.2 Exercise: Set-Up a Garage Three Bay Shed.

#### Task:


Set up a program for a **Three Bay Horse Shed**. Each of the Horse Sheds 1, 2 and 3 have an individual Manual Switch S1, S2 and S3 that turns on/off a Light/Heater within each shed, provided that the Photo Cell indicates that it is dark outside. A Manual override switch (S4) is used to Manually turn on all the Sheds Lights/Heaters irrespective if its Day or Night time.

**Note the Result is provided below but one should try this without looking at the result.**

#### What to Do:

- Design and Debug software for a Three Bay Horse Shed.
- Save the program as **Three Bay Horse Shed** and download it to the CPU.
- Debug and Test the **Three Bay Horse Shed** program.

#### Result:

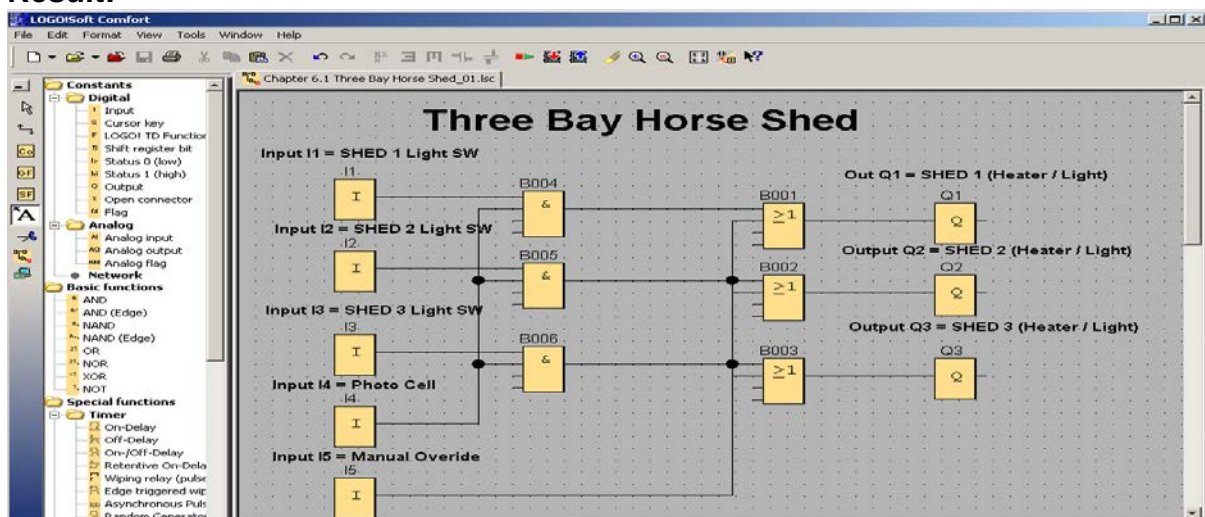

THREE BAY HORSE SHED CONTROL PROGRAM

---

## 2.7 Check what you've learnt this Chapter

### I Know:

- ⇒ How to Program a Siemens LOGO PLC using FBD Format.
- ⇒ What a normally open "NO" and normally closed "NC" contacts are used for.
- ⇒ I understand when to use "AND" or "OR" gate logic.
- ⇒ I understand when to use an "AND" before "OR" gate logic.
- ⇒ I understand when to use an "OR" before "AND" gate logic
- ⇒ How a Motor Start / Stop circuit operates and how it is programmed.

### I Can:

- ⇒ Program a Siemens LOGO using FBD format.
- ⇒ Understand when to used a normally open "NO" or normally closed "NC" contacts in the User Software.
- ⇒ Understand when to use "AND" or "OR" gate logic.
- ⇒ Understand when to use an "AND" before "OR" gate logic.
- ⇒ Understand when to use an "OR" before "AND" gate logic
- ⇒ Understand how a Motor Start / Stop software is programmed.